

Willis Allstead

CPE 201L


Section: 1102

Deepak Tosh


May 3, 2016

### LAB 11: Counters

Work:

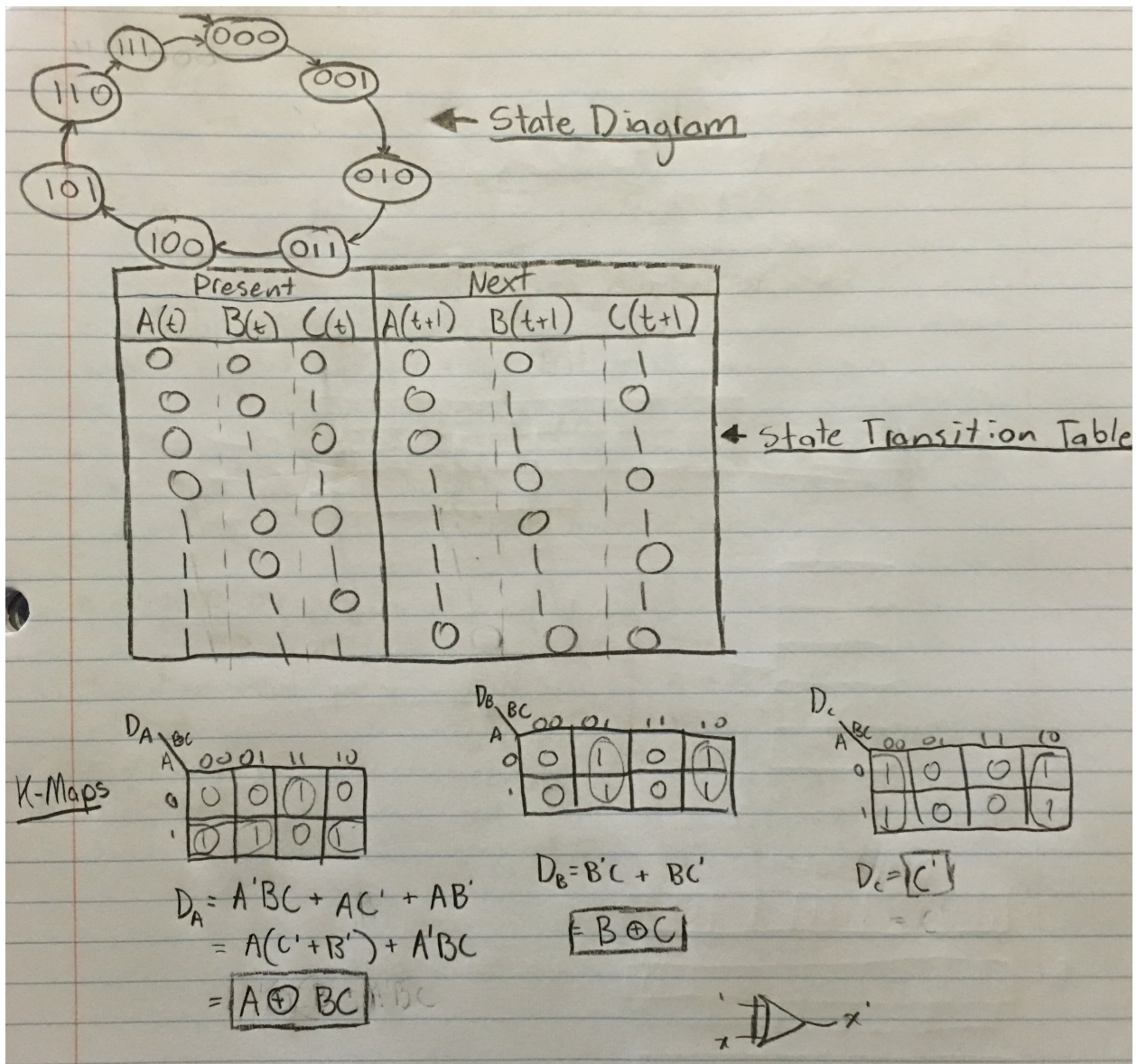

in Logism:

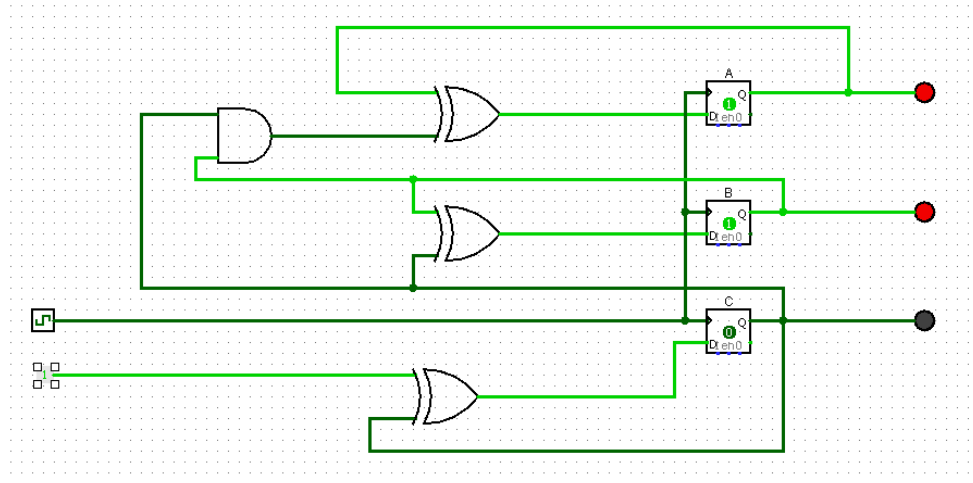

On breadboard:

